
My Experiments in Building Bitx

Dr.Sunil Thomas T, VU2SWX


Principal
College of Engineering Attingal
suniltt@gmail.com

December 18, 2016

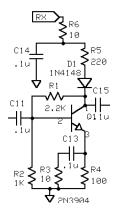
Basic building block: A broad band amplifier



Bidirectional Amplifier

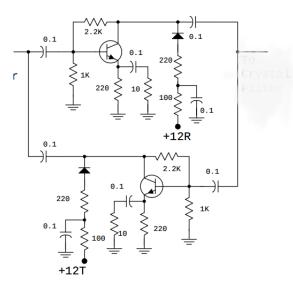


Bitx Block Diagram

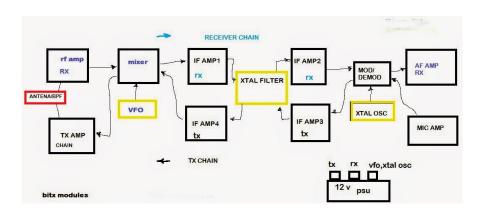



Schematic Diagram

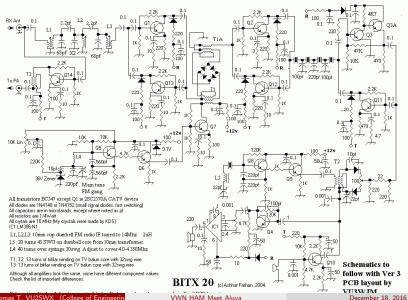

Where to innovate and improve

- Bi-directional amplifiers
- Crystal Filter
- Mixer
- Band pass filter
- VFO Band conversion



How to build

- Buy a populated board from the designer
- Buy a PCB from ebay and build
- Build it in ugly style

Some of my builds Ugly style 40m






Some of my builds Ugly style 40m




Some of my builds Manhattan style 40m.

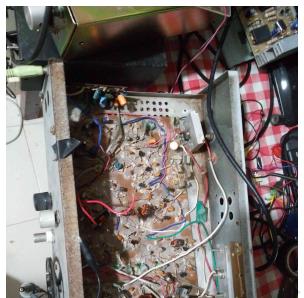




Some of my builds: ON PCB 20m

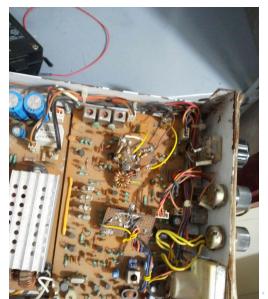

Some of my builds On PCB with BEL Filter



Some of my builds HFI 14 PCB 40m

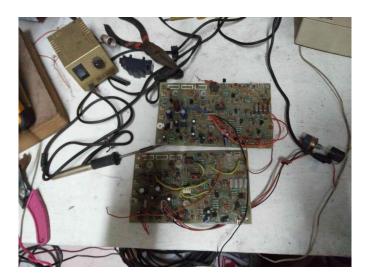

Some of my builds: Manhattan style 80m



My current shack



Contact me

http://brainstorms.in Email vu2swx@gmail.com



Thanks to Lord Dinkan



